

**DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/MANAGEMENT/  
COMMERCIAL PRACTICE, NOVEMBER - 2025**

**DIGITAL ELECTRONICS & MICROPROCESSORS**

[Maximum marks: 100]

[Time: 3 Hours]

**PART – A**

**Maximum marks: 10**

**I.** (Answer *all* the questions in one or two sentences. Each question carries **2** marks)

1. What is propagation delay?
2. What is K-map?
3. Define decoder.
4. Define modulus of a counter.
5. List any four addressing modes of a microprocessor. (5 x 2 = 10)

**PART – B**

**Maximum marks: 30**

**II.** (Answer any *five* of the following questions. Each question carries **6** marks)

1. Explain the basic gates using the truth table.
2. Explain half adder with a truth table.
3. State and explain De-morgans theorem.
4. Simplify the following expression using K-map for four variables A,B,C,D.  
$$Y = M1+M3+M5+M7+M9+M12+M13$$
5. List any six applications of counters.
6. List any six features of a microprocessor.
7. Explain the logical instructions in the microprocessor. (5 x 6 = 30)

**PART – C**

**Maximum marks: 60**

(Answer *one full* question from each unit. Each full question carries **15** marks)

**UNIT – I**

**III.** (a) Implement the logic gates for the following expressions.

(i)  $(A+B)(C+D+E)$       (ii)  $(A+\bar{B} +C)(D+\bar{E})$  (7)

(b) Draw the symbols and truth table of the following logic gates.

(i) NAND (ii) EX-OR (iii) NOR (iv) EX-NOR (8)

**OR**

- IV.** (a) Explain any two logic families with advantages. (8)  
(b) What is 1's complement and 2's complement of a binary number.  
Also write 1's complement and 2's complement of 1010101. (7)

**UNIT - II**

- V.** (a) Draw and explain 1X 4 demultiplexer. (8)  
(b) Draw the logic circuit and give the truth table of full adder using two half adders. (7)

**OR**

- VI.** (a) Explain the working of D Flip flop with diagram and truth table. (8)  
(b) With logic diagram and truth table explain the working of four line to one line multiplexer. (7)

**UNIT - III**

- VII.** (a) Explain any two types of shift registers with neat diagram. (8)  
(b) Compare synchronous and asynchronous counters. (7)

**OR**

- VIII.** (a) With neat diagram explain two bit ripple up counter. (8)  
(b) Explain R-2R DAC with neat diagram. (7)

**UNIT - IV**

- IX.** (a) Draw the pin diagram of 8085 microprocessor. (8)  
(b) Explain the instruction set of 8085 microprocessor. (7)

**OR**

- X.** (a) Draw the architecture of 8085. (7)  
(b) Explain the addressing modes of 8085. (8)

-----